

LEMBAR KERJA SISWA
MODUL RANGKAIAN RESISTOR
Kamis, 29 April 2010 Kelas X
PELAJARAN KE-1

No.	R_1	R_2	Serial Ekivalen	Paralel Ekivalen
1	2	4		
2	3	6		
3	3	8		
4	4	6		
5	4	10		
6	5	12		
7	10	12		
8	10	15		
9	12	18		
10	12	16		
11	12	24		
12	12	36		
13	10	30		
14	12	54		
15	30	34		
16	15	20		
17	15	25		
18	20	24		
19	28	24		
20	28	36		
21	30	32		
22	30	34		
23	30	36		
24	12	48		
25	12	60		
26	20	30		
27	21	49		
28	21	28		
29	28	54		
30	30	42		
31	42	60		
32	42	49		
33	34	56		
34	56	64		

LEMBAR KERJA SISWA
MODUL RANGKAIAN RESISTOR
Kamis, 29 April 2010 Kelas X
PELAJARAN KE-2

No.	R_1	R_2	R_3	Serial Ekivalen	Paralel Ekivalen
1	2	4	8		
2	3	6	12		
3	3	8	12		
4	4	6	16		
5	4	10	12		
6	5	12	24		
7	10	12	20		
8	10	15	30		
9	12	18	24		
10	12	16	36		
11	12	24	48		
12	12	36	48		
13	10	30	60		
14	12	54	24		
15	30	34	17		
16	15	20	40		
17	15	25	60		
18	20	24	60		
19	28	24	48		
20	28	36	42		
21	30	36	48		
22	30	34	42		
23	30	36	48		
24	12	48	56		
25	12	60	54		
26	20	30	70		
27	21	49	70		
28	21	28	56		
29	28	54	72		
30	30	42	48		
31	20	80	30		
32	42	49	17		
33	34	56	28		
34	56	64	28		

LEMBAR KERJA SISWA
MODUL RANGKAIAN RESISTOR
Kamis, 29 April 2010 Kelas X
PELAJARAN KE-3

No.	R_1	R_2	R_3	R_4	Serial Ekivalen	Paralel Ekivalen
1	2	4	12	8		
2	3	6	18	24		
3	3	8	24	16		
4	4	6	20	24		
5	4	10	8	12		
6	5	12	16	20		
7	10	12	18	24		
8	10	15	20	30		
9	12	18	30	27		
10	12	16	24	28		
11	12	24	36	48		
12	12	36	14	56		
13	10	30	18	54		
14	12	54	32	6		
15	30	34	27	63		
16	15	20	25	75		
17	15	25	35	90		
18	20	24	28	72		
19	28	24	12	81		
20	28	36	8	18		
21	30	32	27	63		
22	30	34	32	48		
23	30	36	32	40		
24	12	48	8	36		
25	12	60	6	15		
26	20	30	10	50		
27	21	49	28	56		
28	21	28	42	49		
29	28	54	45	63		
30	30	42	14	56		
31	42	60	14	72		
32	42	49	56	14		
33	34	56	63	68		
34	56	64	72	48		